

CS 4341
Fall 2019
Assigned: February 6th, 2019
Homework 2
Due: March 1st, 2019 11:59 pm

Objective:

Complete the following Exercises from the Mano book.

For the written exercises and diagrams:


- Turn in a PDF file to the blackboard in the form of <COHORTNAME>.HW2.PDF.

For the Program and output, the following should be turned in:

- The program in the form of <COHORTNAME>.Program2.<EXTENSION>
- An output file as a text file, not a screen capture, in the form of <COHORTNAME>.Output2.txt.

 Problem 1: Read a Circuit (10 points) Vishal

Given this circuit, find the formulas for T1, T2, T3, T4, F1, and F2.



- $T1 = B' \cdot C$
- $T2 = A' \cdot B$
- $T3 = A + (B' \cdot C)$
- $T4 = (A' \cdot B) \text{ XOR } D = (A' \cdot B)'D + (A' \cdot B)D'$
- $F1 = T3 + T4 = (A + (B' \cdot C)) + ((A' \cdot B)'D + (A' \cdot B)D')$
- $F2 = T2 + D' =$

Problem 2: Normalized Forms (5 points)

Simplify the equations for F_1 and F_2 , resulting in a sum of products normalized form.

F_1

A	B	C	D	$B'C$	$A+B'C$	$A'B$	$(A'B)'D+(A'B)D'$	$(A+B'C)+(A'B)'D+(A'B)D'$
0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1	1
0	0	1	0	1	1	0	0	1
0	0	1	1	1	1	0	1	1
0	1	0	0	0	0	1	1	1
0	1	0	1	0	0	1	0	0
0	1	1	0	0	0	1	1	1
0	1	1	1	0	0	1	0	0
1	0	0	0	0	1	0	0	1
1	0	0	1	0	1	0	1	1
1	0	1	0	1	1	0	0	1
1	0	1	1	1	1	0	1	1
1	1	0	0	0	1	0	0	1
1	1	0	1	0	1	0	1	1
1	1	1	0	1	1	0	0	1
1	1	1	1	0	1	0	1	1

F_1

AB \ CD	00	01	11	10
00	0	1	1	1
01	1	0	0	1
11	1	1	1	1
10	1	1	1	1

$$F_1 = A + B'D + B'C + BD'$$

F_2

A	B	C	D	$(A'B)$	D'	$(A'B)+D'$
0	0	0	0	0	1	1
0	0	0	1	0	0	0
0	0	1	0	0	1	1
0	0	1	1	0	0	0
0	1	0	0	1	1	1
0	1	0	1	1	0	1
0	1	1	0	1	1	1
0	1	1	1	1	0	1
1	0	0	0	0	1	1
1	0	0	1	0	0	0
1	0	1	0	0	1	1
1	0	1	1	0	0	0
1	1	0	0	0	1	1
1	1	0	1	0	0	0
1	1	1	0	0	1	1
1	1	1	1	0	0	0

F_2

AB \ CD	00	01	11	10
00	1	0	0	1
01	1	1	1	1
11	1	0	0	1
10	1	0	0	1


$$F_2 = D' + A'B$$

Problem 3: Draw Circuits (5 points)


Draw a new circuit for F1 and F2

Circuit 1

$$F_1 = A + B'D + B'C + BD'$$

 

$$F_2 = D' + A'B$$

 

Problem 4: Circuit Design (5 points)

Design a combinational circuit with four input bits and one output bit. Show the truth table, the normalized equation, and the circuit. This includes gates, encoders, decoders, multiplexers, arbiters, adders, and half-adders.

Solve: The output is 1 when the binary value of the inputs is an odd number.

4) Circuit

A -
B -
C -
D -
output

$$F = D$$

This is because a binary # is odd if it ends in a '1'.

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

AB \ CD	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	0	1	1	0
10	0	1	1	0



Alternating

$$F = D$$

  Problem 5: Circuit Design (5 points)

Design a combinational circuit with four input bits and one output bit. Show the truth table, the normalized equation, and the circuit. This includes gates, encoders, decoders, multiplexers, arbiters, adders, and half-adders.

Solve: The output is 1 when the binary value of the inputs is less than 10. The output is 0 otherwise.




Truth Table

A	B	C	A'	B'	C'	ABC'	A + ABC'
0	0	0	1	1	1	0	1
0	0	1	1	1	0	0	1
0	1	0	1	0	1	0	1
0	1	1	1	0	0	0	1
1	0	0	0	1	1	1	1
1	0	1	0	1	0	0	0
1	1	0	0	0	1	0	0
1	1	1	0	0	0	0	0

 Problem 6: The Seven Segment Decoder (25 points)

A Binary-Number to a Seven Segment decoder is a combinational circuit that converts a decimal value to an appropriate code for the selection of segments in the indicator used to display the decimal digit in a familiar form. The seven outputs of the decoder (a, b, c, d, e, f, g) select the corresponding segments in the display. Using a truth table of 4 input bits, design a circuit that will run the seven segment encoder. Values 10 through 15 should not be included.



(a) Segment designation




(b) Numerical designation for display

Question 6: Seven Segment Encoder

Truth Table

Input				Output							
A	B	C	D		a	b	c	d	e	f	g
0	0	0	0	(0)	1	1	1	1	1	1	0
0	0	0	1	(1)	0	1	1	0	0	0	0
0	0	1	0	(2)	1	1	0	1	1	0	1
0	0	1	1	(3)	1	1	1	1	0	0	1
0	1	0	0	(4)	0	1	1	0	0	1	1
0	1	0	1	(5)	1	0	1	1	0	1	1
0	1	1	0	(6)	1	0	1	1	1	1	1
0	1	1	1	(7)	1	1	1	0	0	0	0
1	0	0	0	(8)	1	1	1	1	1	1	1
1	0	0	1	(9)	1	1	1	1	0	1	1


Don't
Cares
10-15

 

NOTE: The box seen above is the DECODER

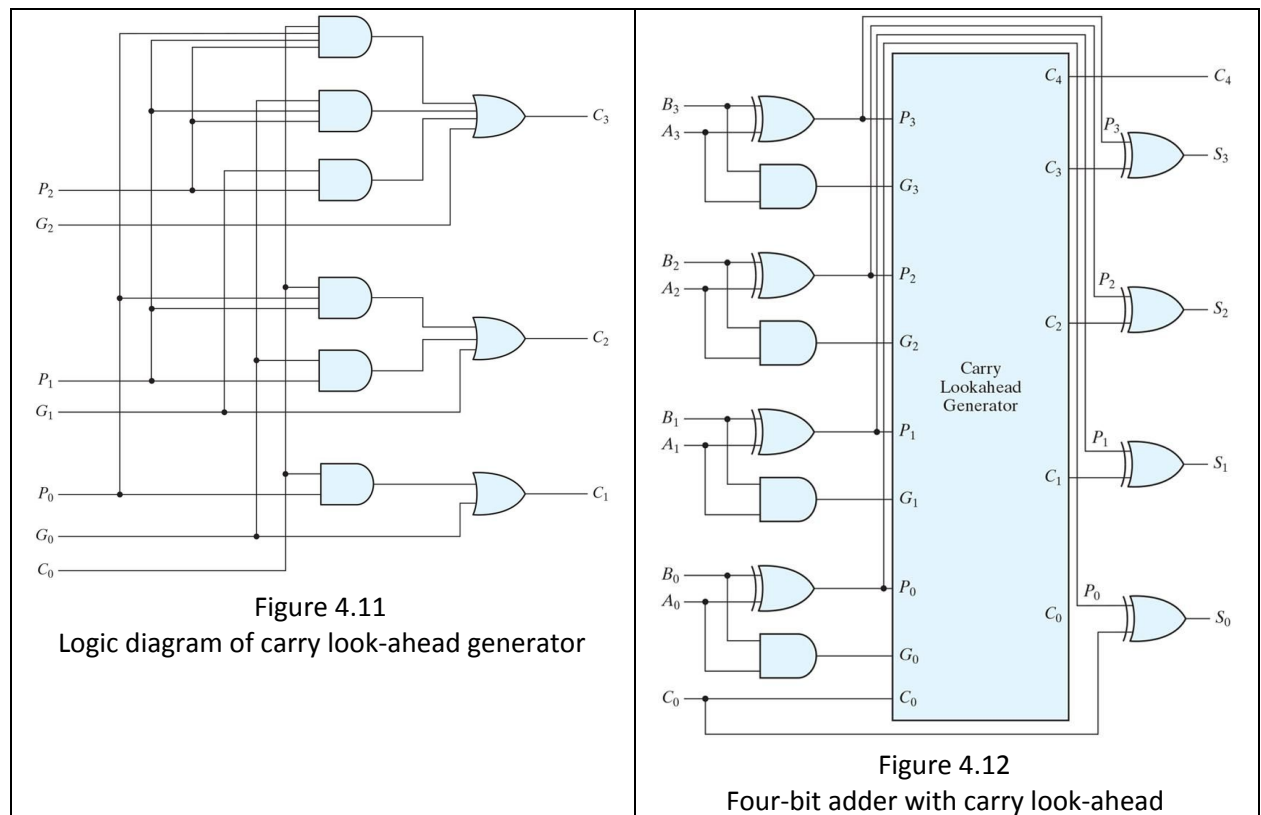Problem 7: Delays (5 points)

Assume the XOR gates have a delay of 10 ns, AND gates have a delay of 5 ns, and OR Gates have a delay of 5 nanoseconds. What is the total delay in the four-bit adder with carry look-ahead? Hint: Look for the longest path through **both** circuits. This is a problem about being able to read a diagram and think through the problem. (Most students just freak out at the sight of a large circuit. Please breathe).



30 Nanosecond Delay


10 ns (XOR GATE Delay) + 5 ns (AND GATE Delay) + 5 ns (OR GATE Delay) + 10 ns (XOR Gate Delay) = 30 ns

Problem 8: Multiplexer 1 (5 points)


Implement the following Boolean function with a 4-bit multiplexer.

$$F(A,B,C,D) = \sum (0, 2, 5, 8, 10, 14)$$

 e) $F(A,B,C,D) = \sum (0, 2, 5, 8, 10, 14)$



A	B	C	D	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

 


Problem 9: Multiplexer 2 (10 points)

Implement the following Boolean function with a **3-bit multiplexer** and appropriate gate logic.

$$F(A,B,C,D) = \prod (1,3,4,6,7,9,11,12,13,15)$$

A	B	C	D	F	
0	0	0	0	1	F = D'
0	0	0	1	0	
0	0	1	0	1	F = D'
0	0	1	1	0	
0	1	0	0	0	F = D
0	1	0	1	1	
0	1	1	0	0	F = 0
0	1	1	1	0	
1	0	0	0	1	F = D'
1	0	0	1	0	
1	0	1	0	1	F = D'
1	0	1	1	0	
1	1	0	0	0	F = 0
1	1	0	1	0	
1	1	1	0	1	F = D'
1	1	1	1	0	

 

Hardware Programming Language (Verilog, etc.) (25 points)


Write the HDL gate-level hierarchical description of a four-bit adder-subtractor for unsigned binary numbers similar to the following circuit. Be sure to examine the sample code on the next page.

Figure 4.13a, 4-Bit adder-subtractor without overflow.

Inputs: 4-Bit A, 4-Bit B, and Mode M (0=add/1=subtract)

Interfaces: Carry Bits C1, C2, C3

 Outputs: Carry C (1 Bit, C4) , Sum S (4 bit)



Example Code:

What is special about this code is the system is now using *arrays* of components and bits in Verilog. This is a sample for you to study to use as a base to complete the program, not the program itself. Combine the sample code with the diagram to complete the problem

```
module Add_half (input a, b, output c_out, sum);  
    xor G1(sum, a, b);      // Gate instance names are optional  
    and G2(c_out, a, b);  
endmodule
```

```
module Add_full (input a, b, c_in, output c_out, sum);      // See Fig. 4.8  
    wire w1, w2, w3;      // w1 is c_out; w2 is sum  
    Add_half M1 (a, b, w1, w2);  
    Add_half M0 (w2, c_in, w3, sum);  
    or (c_out, w1, w3);  
endmodule
```

```
module Add_rca_4 (input [3:0] a, b, input c_in output c_out, output [3:0] sum);  
    wire c_in1, c_in3, c_in3, c_in4;      // Intermediate carries  
    Add_full M0 (a[0], b[0], c_in, c_in1, sum[0]);  
    Add_full M1 (a[1], b[1], c_in1, c_in2, sum[1]);  
    Add_full M2 (a[2], b[2], c_in2, c_in3, sum[2]);  
    Add_full M3 (a[3], b[3], c_in3, c_out, sum[3]);  
endmodule
```

```
module Add_rca_8 (input [7:0] a, b, input c_in, output c_out, output [7:0] sum,)   
    wire c_in4;  
    Add_rca_4 M0 (a[3:0], b[3:0], c_in, c_in4, sum[3:0]);  
    Add_rca_4 M1 (a[7:4], b[7:4], c_in4, c_out, sum[7:4]);  
endmodule
```